

Student Exercise Core

1. A 12V power supply is connected to a $3\text{k}\Omega$ resistor. What is the current flowing in the circuit?

$$I = \frac{V}{R} = \frac{12}{3 \times 10^3} = 4 \text{ mA}$$


2. A 9V battery provides a current of 1.5A to a resistor, What is the value of the resistance?

$$R = \frac{V}{I} = \frac{9}{1.5} = 6 \Omega$$


3. A resistor of 15Ω is connected to a battery of unknown voltage. The current in the circuit is measured to be 0.1A. What is the voltage of the battery?

$$V = I \times R = 15 \times 0.1 = 1.5 \text{ V}$$

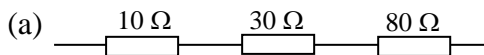
4. Find the total resistance in each of the following combinations of resistors.



$$10 + 30 + 80 = 120 \Omega$$

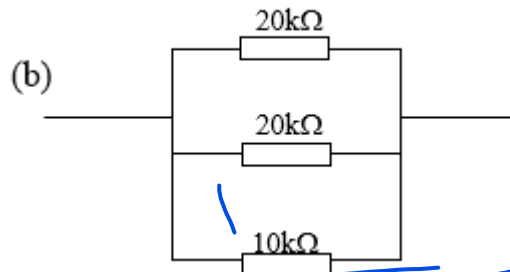

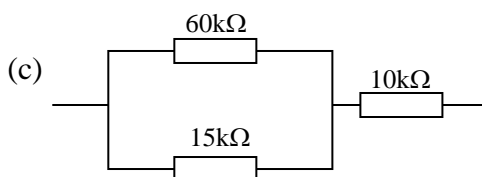
$$\frac{1}{20} + \frac{1}{20} + \frac{1}{10} = 5 \text{ k}\Omega$$



$$12 \text{ k} + 10 \text{ k} = 22 \text{ k}\Omega$$

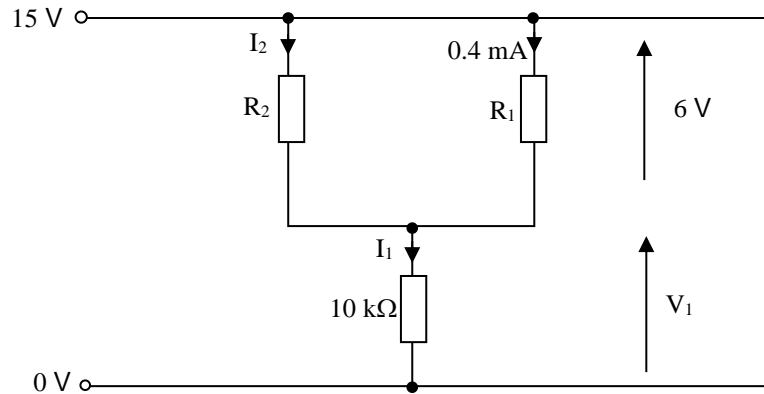5. Determine the values of R_1 , V_1 , I_1 , I_2 and R_2 in the following circuit.



(a) $R_1 = \frac{V}{I} = \frac{6}{0.4 \times 10^{-3}} = 15 \text{ k}\Omega$

(b) $V_1 = 15 - 6 = 9 \text{ V}$

(c) $I_1 = \frac{V}{R} = \frac{9}{10 \text{ k}} = 900 \mu\text{A}$


(d) $I_2 = 900 \mu\text{A} - 0.4 \text{ mA} = 500 \mu\text{A}$

(e) $R_2 = \frac{6}{500 \mu\text{A}} = 12 \text{ k}\Omega$

(f) What is the power dissipated in R_1 ?
 $P = I \times V = 0.4 \text{ mA} \times 6 \text{ V} = 2.4 \text{ mW}$

or $\frac{V^2}{R} = \frac{6^2}{15 \text{ k}} = 2.4 \text{ mW}$

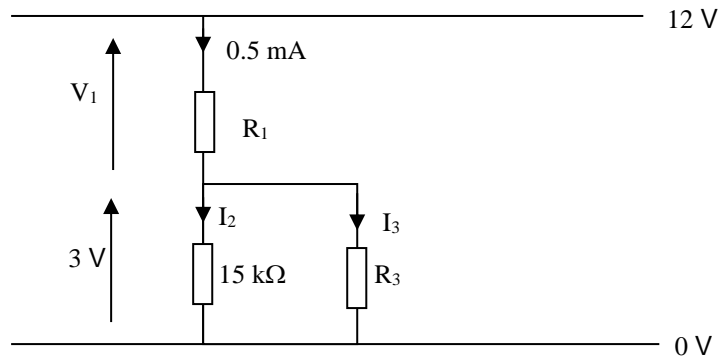6. Determine the values of V_1 , R_1 , I_2 , I_3 and R_3 in the following circuit. Hence determine the power dissipated in the $15\text{k}\Omega$ resistor.



(a) V_1 $12 - 3 = 9\text{ V}$

(b) $R_1 = \frac{V}{I} = \frac{9}{0.5\text{ mA}} = 18\text{ k}\Omega$

(c) $I_2 = \frac{V}{R} = \frac{3}{15\text{ k}} = 200\text{ }\mu\text{A}$


(d) $I_3 = 0.5\text{ mA} - 200\text{ }\mu\text{A} = 300\text{ }\mu\text{A}$

(e) $R_3 = \frac{V}{I} = \frac{3\text{ V}}{300\text{ }\mu\text{A}} = 10\text{ k}\Omega$

- (f) What is the power dissipated in the $15\text{k}\Omega$ resistor.

$\frac{V^2}{R} = \frac{3^2}{15\text{ k}} = 600\text{ }\mu\text{W}$

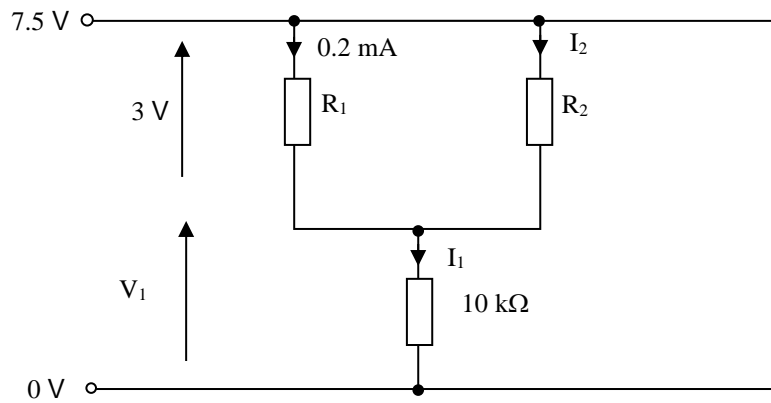7. Determine the values of V_1 , I_1 , I_2 , R_1 , and R_2 in the following circuit.



(a) V_1 $7.5 - 3 = 4.5V$

(b) I_1 $\frac{V}{R} = \frac{4.5}{10k} = 450\mu A$

(c) I_2 $450\mu A - 0.2mA = 250\mu A$


(d) R_1 $\frac{V}{I} = \frac{3}{0.2mA} = 15k\Omega$

(e) R_2 $\frac{3}{250\mu A} = 12k\Omega$

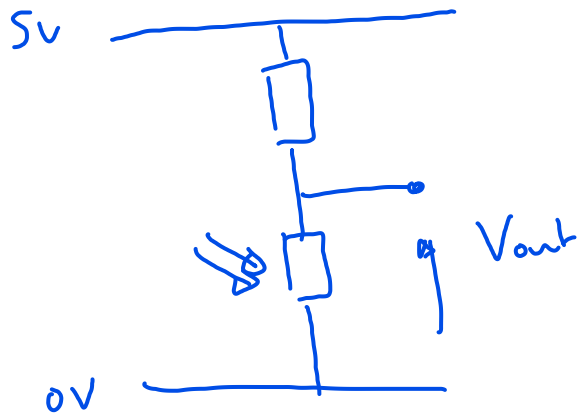
- (f) What is the effective resistance of R_1 and R_2 in parallel?

$\frac{1}{\frac{1}{12k} + \frac{1}{15k}} = 6.67k\Omega$


Draw a light sensing circuit where the output voltage falls with increasing illumination?



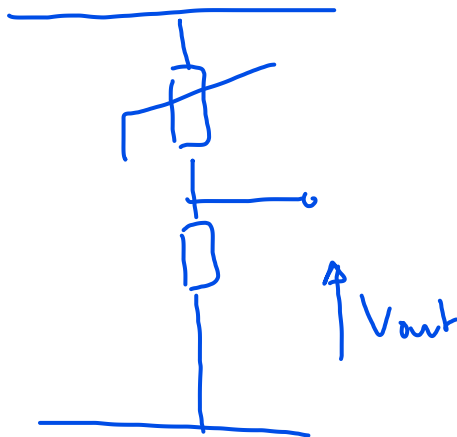Draw a Temperature sensor where the output rises as it gets hotter?



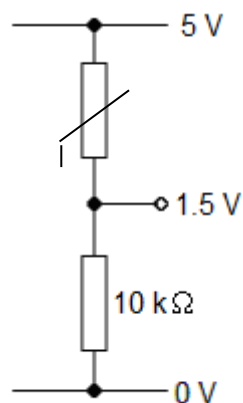
Calculate the Thermistor resistance value



$$I = \frac{V}{R} = \frac{1.5}{10k} = 150 \mu A$$

$$R = \frac{V}{I} = \frac{5 - 1.5}{150 \mu A} = 23.3 k\Omega$$

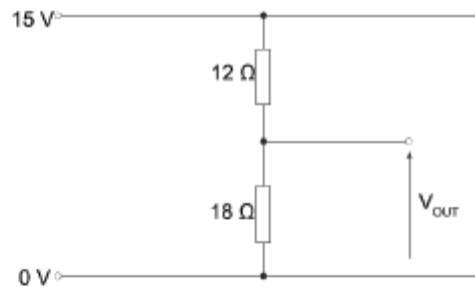7. Thevenin's theorem is used to produce an equivalent circuit for the voltage divider circuit shown.




- (a) Calculate the values of V_{oc} and R_{eq} .

$$V_{oc} = \frac{18}{12+18} \times 15 = 9V$$

$$I_{sc} = \frac{15}{12\Omega} = 1.25A$$

$$R_{Eqw} = \frac{V_{oc}}{I_{sc}} = \frac{9}{1.25} = 7.2\Omega$$

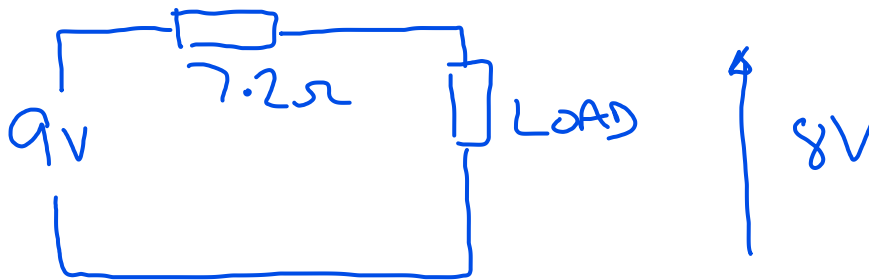- (b) (i) Draw the equivalent circuit with a load resistance connected across the output terminals.



- (ii) Use the equivalent circuit to calculate the maximum permissible load current to ensure the output voltage V_{OUT} does not fall below 8.0 V.

$$\therefore V_{across\ 7.2\Omega} = 9 - 8 = 1V$$

$$I = \frac{V}{R} = \frac{1}{7.2} = \frac{5}{36} A \ (138.9mA)$$

$$R = \frac{V}{I} = \frac{8}{138.9mA} = 57.6\Omega$$